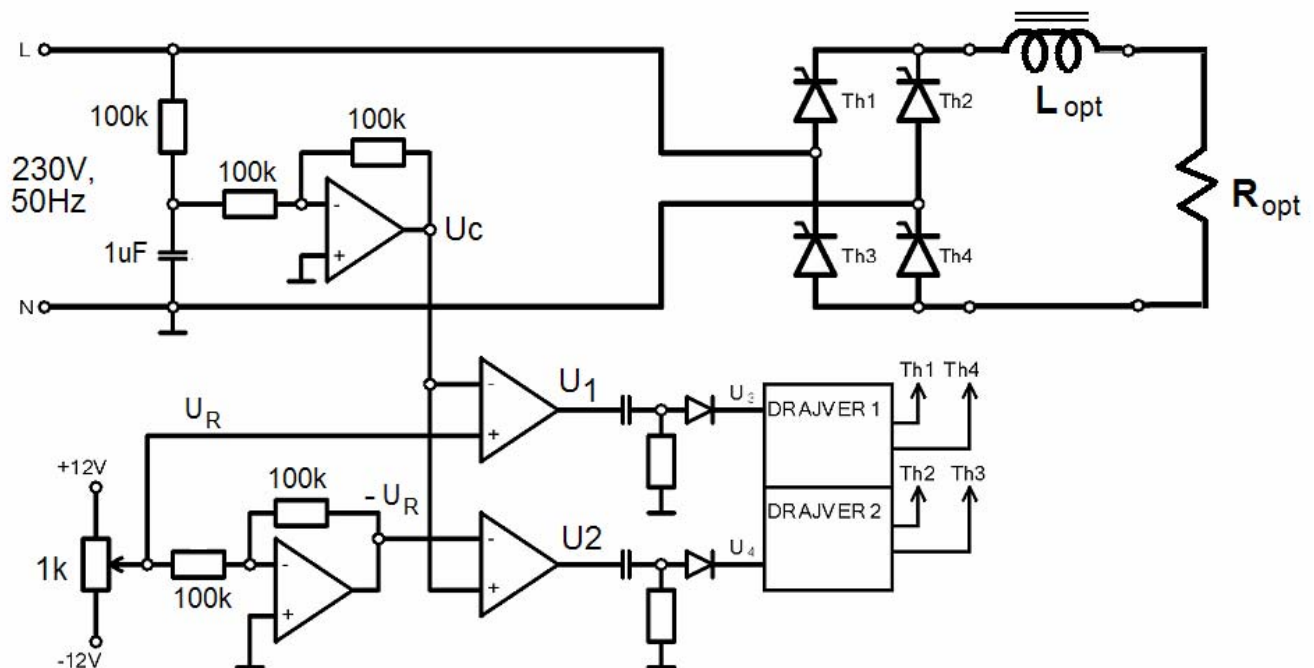


VISER-NET-SPECIJALISTIČKE STUDIJE

PREDMET: Upravljanje Elektroenergetskim Pretvaračima

DOMAĆI ZADATAK_16


Za energetska kolo ispravljača na slici, nacrtati za vrednosti ugla upravljanja $\alpha = 0^\circ, 90^\circ, 120^\circ$, karakteristične talasne oblike: napon na izlazu iz ispravljača, struje tiristora Th1-Th4 i struju koju ispravljač uzima iz mreže. Za upravljačko kolo nacrtati karakteristične talasne oblike signala U_C , U_R , U_1 , U_2 . Odrediti prenosnu karakteristiku U_0/U_C (odnos izlaznog napona U_0 i upravljačkog napona U_R). Takođe odrediti prenosnu karakteristiku – zavisnost ugla upravljanja od upravljačkog napona $\alpha = F(U_R)$. Odrediti opseg promene struje opterećenja u zavisnosti od upravljačkog napona U_R , ako su dati parametri $R_{opt} = 10\Omega$ i $L_{opt} \rightarrow \infty$. Smatrati da su tiristori i diode u ispravljaču idealnih karakteristika.



REŽENJE :

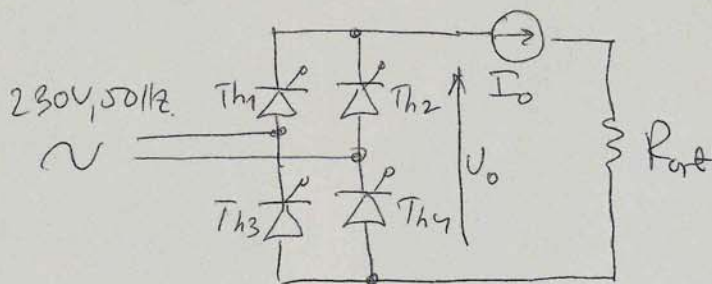(1)

$L_{out} \rightarrow \infty$ induktivnost se ponast kao savršeni ponor i
mora se predstaviti sa strujom I_0




$$I_0 = U_0 / R_{load}$$

$$U_0 = f(d)$$

$d = \text{UCAO u praznoj}$
(fazi nako)

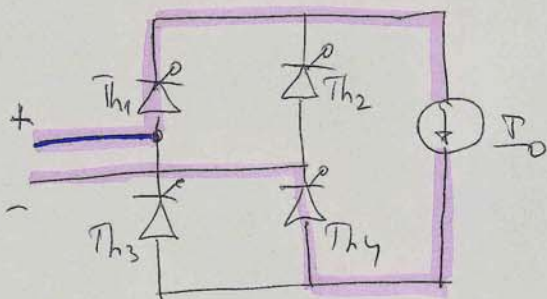
POZITIVNA POLUPERIODA MREŽNOG NAPONA (vode Th_1 i Th_4)



NAPON NA Th_1 , kao i napon
NA Th_4 su jednak ϕ
 $V_{Th1} = V_{Th4} \approx 0$

Th_2 i Th_3 su inverzno
polarizovani. ($V_K > V_A$)

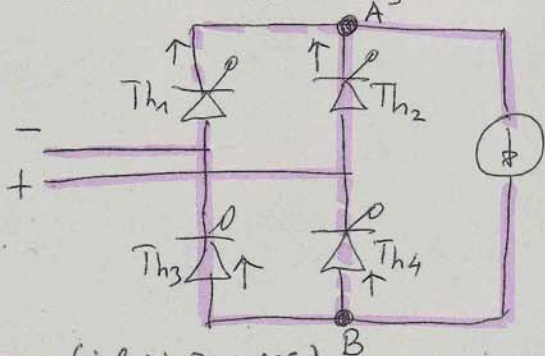
U NEKAKVOJ POLUPERIODI SE ENU USLOV DA PROVEDU
 Th_2 i Th_3 . TO JE POMERANJE I DOVOJ. USLOV, DA
PROVEDU Th_2 i Th_3 . DOVOJAN USLOV JE DA DOVEDENI IMP
ULSE NA REŠT. DRUGEJMA U NEKAKV. POLUPERIODI
POVRATNO Th_2 i Th_3 DOBISA JE SLEDENJE KAO



Uslugu Th_2 inverzno
polarizovano Th_1
u tački A vadi

$$i_{Th1} + i_{Th2} = I_0 = \text{const}$$
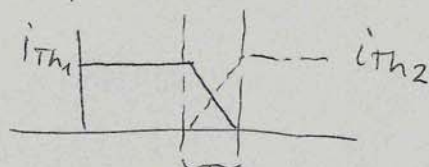
$$i_{Th1} \downarrow \quad i_{Th2} \uparrow$$



Vreme
komutacije
 $\approx 20 \div 50 \mu s$


(izlazi iz vođenja)

Uslugu Th_3 inverzno
polarizovano Th_4


$$i_{Th3} + i_{Th4} = I_0$$

$$i_{Th3} \uparrow \quad i_{Th4} \downarrow$$

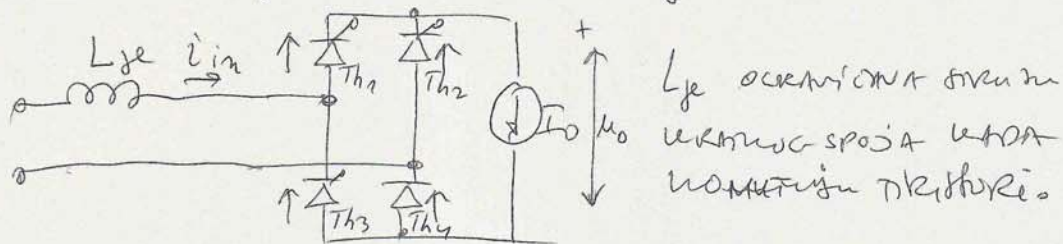U ovom električnom krugu vode se računi (2)
 TIRISTORA, tako da se čeo most može "uvratiti spoj"
 za mrežu. DA bi se ovaj efekt u BUKTIU prena
 mreži se postavlja PRILIKOM L_{je}



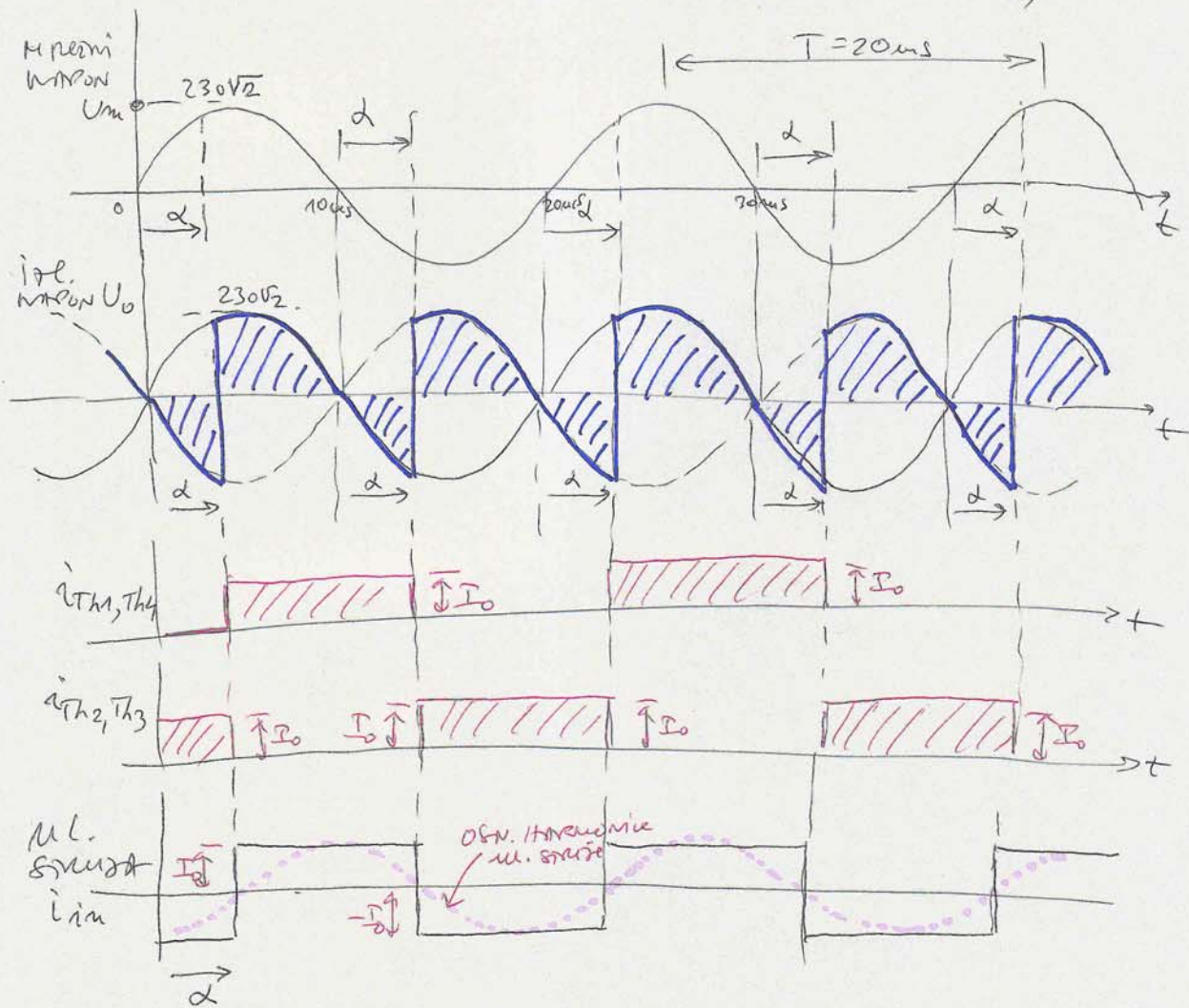
Primeni obliku za MCAO α (pril. vrednost)



Primeni pravilni predu PRVOG HARMONIKA ul. struje i mrežu.
 NAPONA se računa α

1. Zračunavanje relativnog napona (energija napona)

(3)

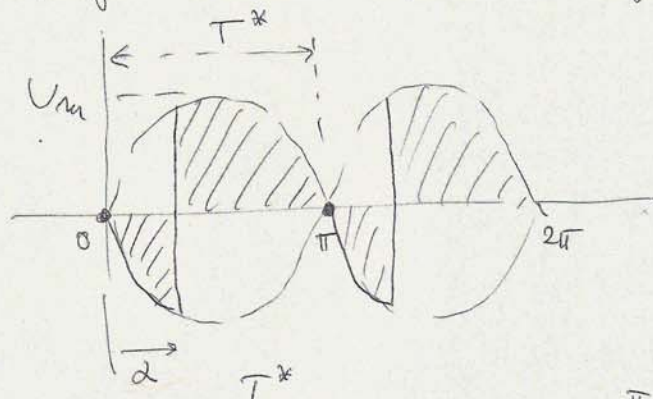

$$T = 20 \text{ ms} \quad f = \frac{1}{T} = 50 \text{ kHz}$$

$$T^* = \frac{T}{2}$$


$$U_{\text{ize sr}} = \frac{1}{T^*} \int_0^{T^*} u_{\text{ize}}(t) \cdot dt = \frac{1}{\frac{\pi}{2}} \int_{\alpha}^{\pi+\alpha} U_m \sin x \, dx$$


$$U_{\text{ize sr}} = \frac{U_m}{\frac{\pi}{2}} \int_{\alpha}^{\pi+\alpha} \sin x \, dx = \frac{U_m}{\frac{\pi}{2}} (-\cos x \Big|_{\alpha}^{\pi+\alpha})$$

$$U_{\text{ize sr}} = \frac{U_m}{\frac{\pi}{2}} (\cos \alpha - \cos(\pi + \alpha)) = \frac{2U_m}{\pi} \cdot \cos \alpha$$

$$U_{\text{ize sr}} = \frac{2\sqrt{2}U}{\pi} \cdot \cos \alpha$$

$$U_{\text{ize}} = f(\alpha)$$


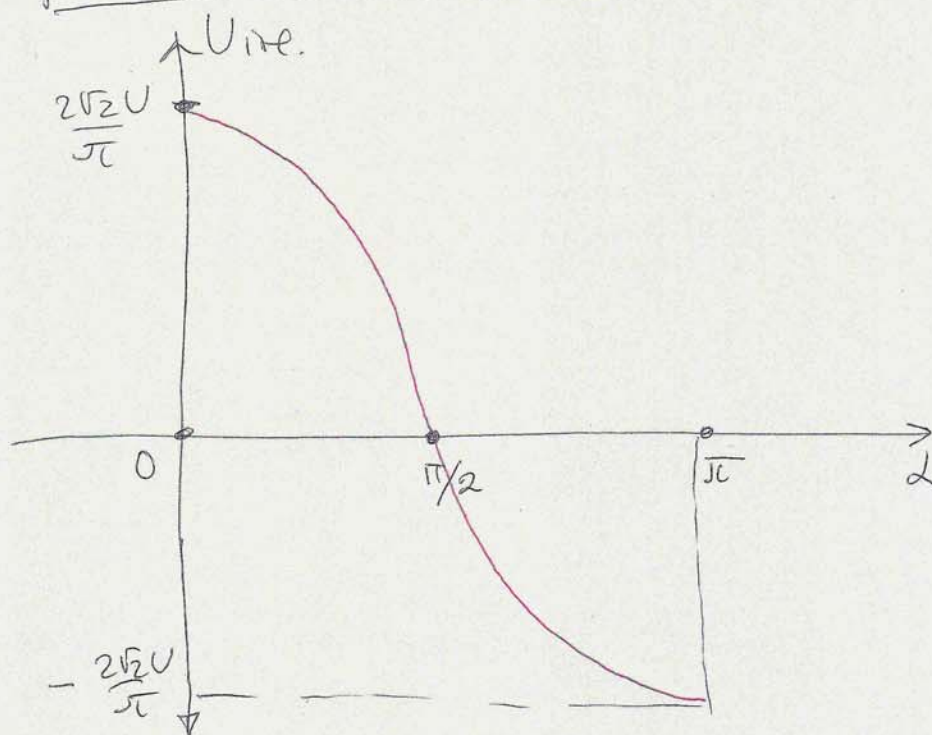


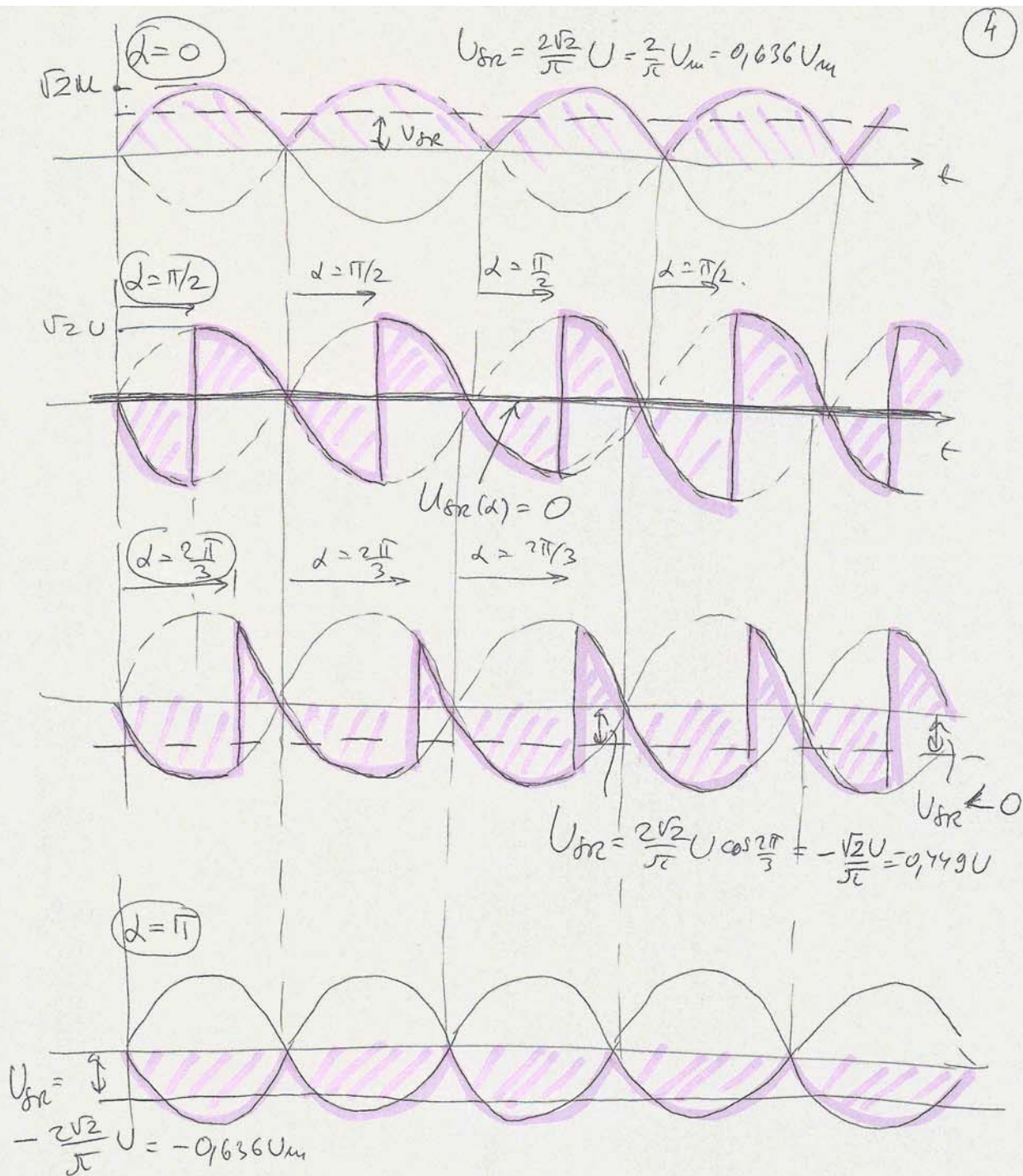


Таблиці зміни середнього напруги та різни напруги
у СА наведено в д.

$$\alpha = 0, \pi/2, \frac{2\pi}{3}, \pi$$

5

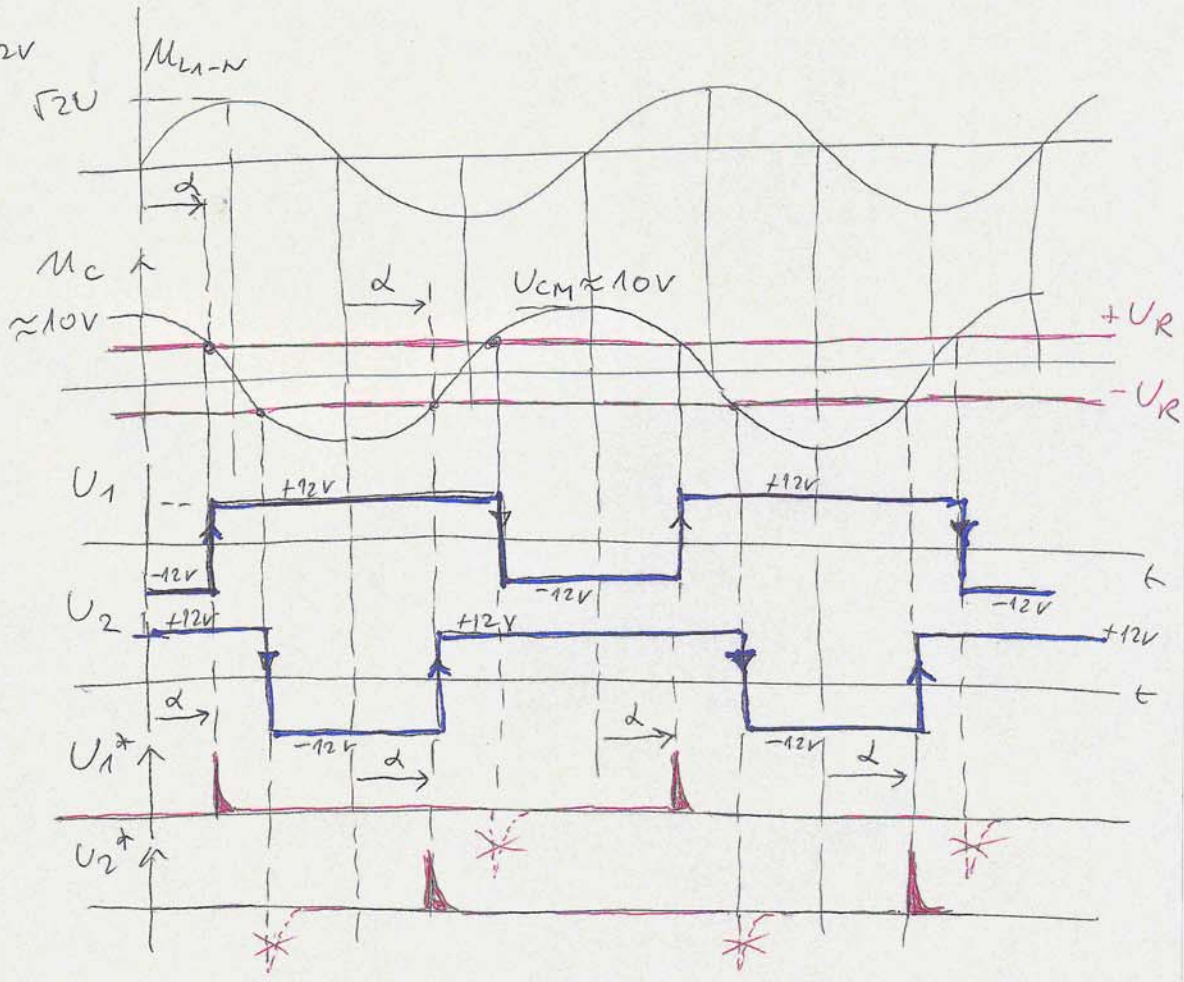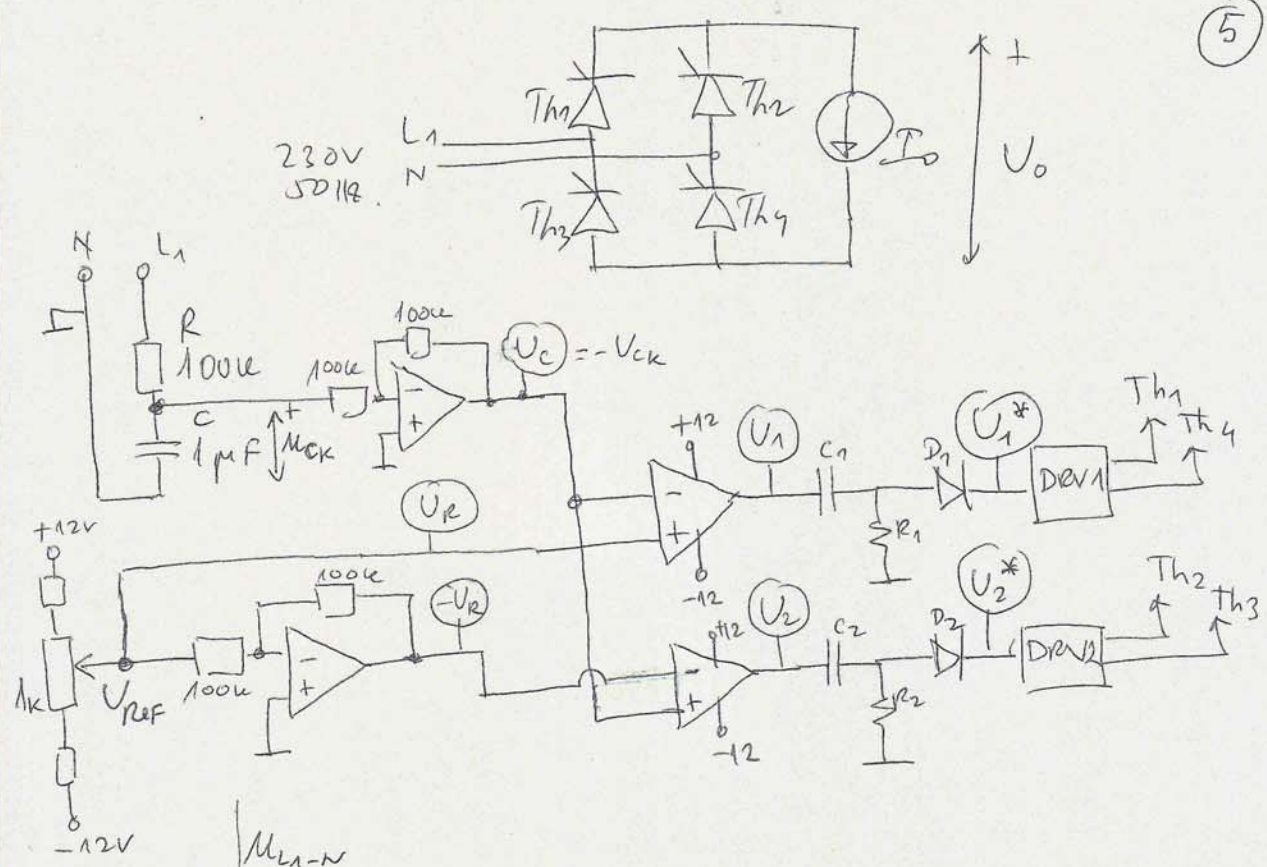

(6)

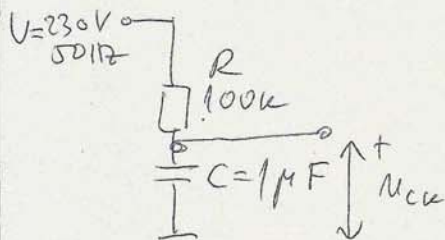

$$\underline{U_{Ck}} = \frac{\underline{U_{L0}}}{\underline{z_1} + \underline{z_2}} \cdot \underline{z_2}$$

$$\underline{U_{Ck}} = \frac{U}{R + \frac{1}{j\omega C}} \cdot \frac{1}{j\omega C}$$

$$\underline{z_1} = R$$

$$\underline{z_2} = \frac{1}{j\omega C}$$

$$\underline{U} = \frac{U}{j\omega CR + 1}$$

$$U_{Ck} = \frac{U}{\sqrt{1 + (\omega CR)^2}}$$

$$\omega = 2\pi \cdot f = 2\pi \cdot 50 = 314 \text{ rad/s}$$

$$C = 1 \cdot 10^{-6} \text{ F}$$

$$R = 100 \cdot 10^3$$

$$\omega CR = 314 \cdot 10^{-6} \cdot 100 \cdot 10^3 = 31,4$$

$$(\omega CR)^2 \gg 1$$

$$U_{Ck} \approx \frac{U}{\omega CR} = \frac{230}{31,4}$$

$$U_{Ck} = 7,32 \text{ V}$$

$$U_{CM} = (\text{MAX. vnešná napávací } U_c)$$

$$U_{CM} = \sqrt{2} \cdot U_{Ck} = 10,3 \text{ V} \approx 10 \text{ V}$$

$$U_{CM} = \frac{U\sqrt{2}}{\sqrt{1 + (\omega CR)^2}} \approx \frac{U\sqrt{2}}{\omega CR} \cdot k$$



Thmode se $U_{REF} = U_R = U_{CM} \cos \alpha \Rightarrow \cos \alpha = \frac{U_R}{U_{CM}}$
 $- U_{REF} = -U_R = U_{CM} \sin \alpha$

$$U_{\text{skrite}} = \frac{2\sqrt{2}U}{\pi} \cos \alpha = \frac{2\sqrt{2}U}{\pi} \cdot \left(\frac{U_R}{U_{CM}} \right)$$

$$U_{\text{skrite}} = \frac{2\sqrt{2}U}{\pi} \cdot \frac{U_R}{U_{CM}} = \frac{2\sqrt{2}}{\pi} \cdot \frac{U}{U_{CM}} \cdot U_R = k \cdot U_R$$

$$k = \frac{2\sqrt{2}}{\pi} \cdot \frac{U}{U_{CM}} = \frac{2\sqrt{2}}{\pi} \cdot \frac{230}{10} = 29,65$$
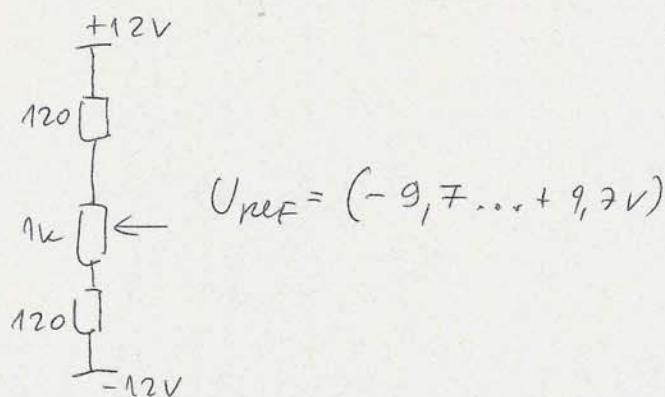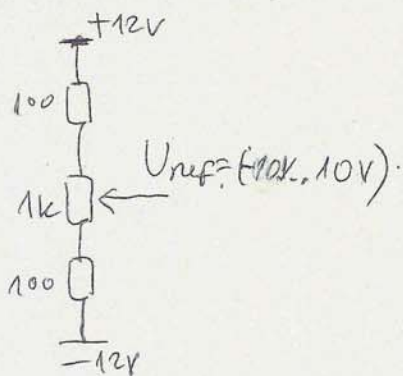
$$U_{\text{skrite}} = 29,65 \cdot U_{REF}$$




1) $U_{REF_{MAX}} = 9,7V \rightarrow \cos \alpha = \frac{U_{R_{MAX}}}{U_{CM}} = \frac{9,7}{10} = 0,97$

оо тде се $\alpha_{min} = 14^\circ (0,24 \text{ rad})$

2) $U_{REF} = 0 \Rightarrow \alpha = \frac{\pi}{2}$

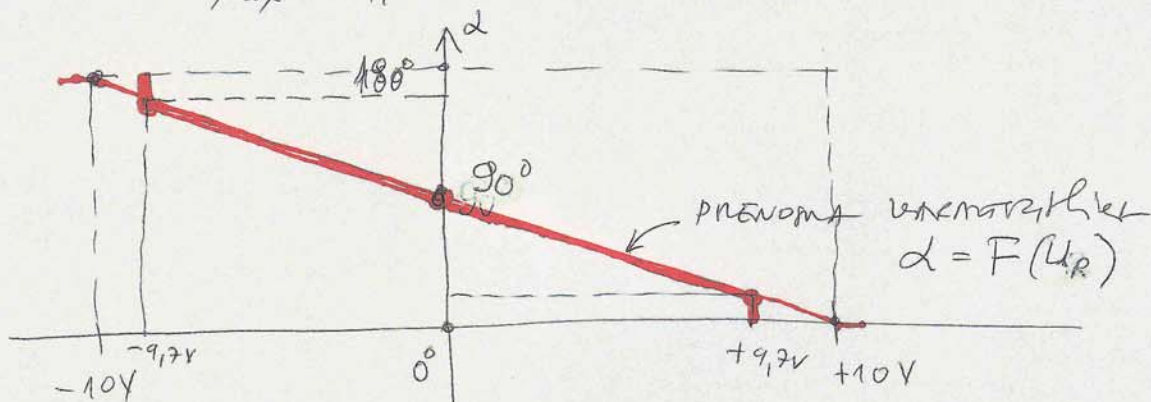3) $U_{REF_{min}} = -9,7V \quad \alpha_{max} = 180^\circ - 14^\circ = 166^\circ (2,89 \text{ rad})$



$14^\circ \leq \alpha \leq 166^\circ$

$U_{SR}^{max}(14^\circ) = \frac{2\sqrt{2}V}{\pi} \cos 14^\circ = 200,4V \Rightarrow I_0 = \frac{200,4V}{10\Omega} = 20A$

$U_{SR}^{min}(166^\circ) = \frac{2\sqrt{2}}{\pi} \cos 166^\circ = -200,4V \Rightarrow I_0 = \frac{-200,4}{10} = -20A$


ОПРЕГ пронеке грмне опрнецак

$-20A \leq I_0 \leq 20A$


НАПОМЕНЕ:

(8)

1) INVERZNIČKI POJAČIVAČ

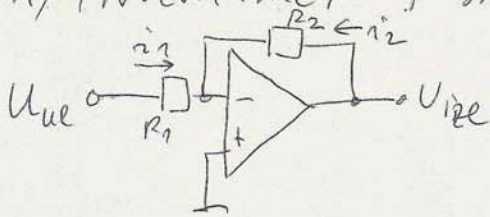
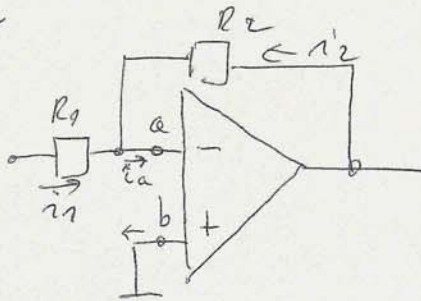
$$\frac{U_{ue}}{R_1} + \frac{U_{ize}}{R_2} = i_a \approx 0$$




za idealni operac.
pojačivač $U_{ab} = 0$ i
struja $i_a = i_b = 0$


$$U_{ize} = -\frac{R_2}{R_1} U_{ue}, \text{ ako je } R_2 = R_1, U_{ize} = -U_{ue}$$

(inverznički
pojačivač
sa pojačanjem
($k_p = -1$))

2) KOMPARATOR

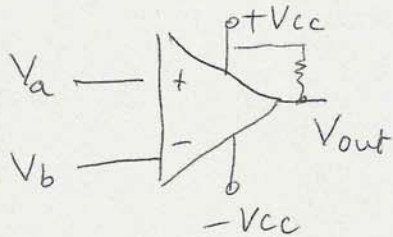

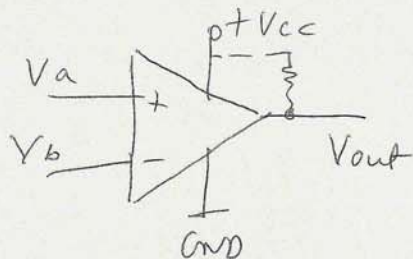
$$\begin{aligned} V_a > V_b & \quad V_{out} = +V_{cc} \\ V_a < V_b & \quad V_{out} = -V_{cc} \end{aligned}$$



$$\begin{aligned} V_a > V_b & \quad V_{out} = +V_{cc} \\ V_a < V_b & \quad V_{out} \approx 0 \end{aligned}$$

(9)

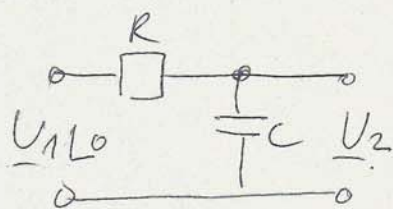

RC
INTEGRATOR

$$\underline{U}_2 = \frac{1}{j\omega RC + 1} \underline{U}_1$$



$\omega RC \gg 1$ (u mren smoren)

$$\underline{U}_2 \approx \frac{1}{j\omega RC} \underline{U}_{1L0} = \frac{1}{j\omega RC} U_1 = \frac{U_1}{\omega RC} \cdot e^{-j\pi/2}$$

$$\underline{U}_2 = -\frac{U_1}{\omega RC} e^{j\pi/2} \quad (\text{obroć fazy na } -\frac{\pi}{2})$$

Proste $u_1 = U_m \sin \omega t \Rightarrow u_2 = -\frac{U_m}{\omega RC} \cos \omega t$


RC Differentiator

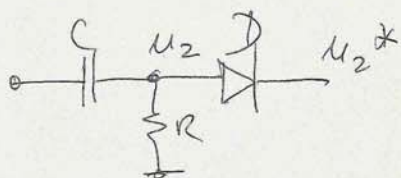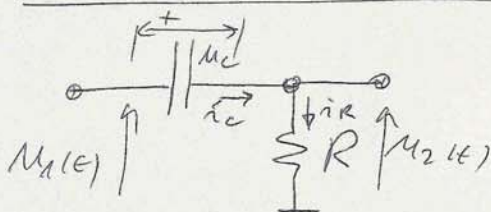

$$u_2 = u_R(t)$$



$$u_2^*$$

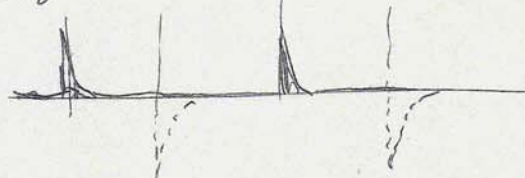

Dioda
przepuszcza
tylko dodatnie
impulsy

