

VISER-MASTER studije ELIN-PE²P 2019/2020

REŠENJA ZADATAKA-I kolokvijum

1.Zadatak

Inteligentni IGBT energetski modul se koristi u AC/AC frekventno regulisanom energetskom pretvaraču. Ulagi mrežni napon je 3x400V, 50Hz. Izgled i osnovne tehničke karakteristike IGBT modula su date u PRILOGU1.


- (a) Nacrtati kompletну električnu šemu pretvarača: mrežni ulaz-ispravljač-LC filter-kolo za početno punjenje banke elektrolita-kolo za kočenje-izlazni invertor-motor
- (b) Odrediti maksimalnu snagu trofaznog asinhronog motora koji se može priključiti na izlaz modula (tačke 4-5-6)
- (c) Projektovati LC filter u jednosmernom DC međukolu, ako je talasnost DC napona <2%, a talasnost DC struje <10%
- (d) Predložiti i projektovati kolo za početno punjenje banke elektrolita; usvojiti da je maksimalna struja punjenja 30A; Podaci za tiristorski modul su dati u PRILOGU2
- (e) Odabrat tip i projektovati ulazne mrežne osigurače
- (f) Dimenzionisati otpornik za kočenje u DC međukolu

2. Zadatak

Za uslove koji su dati u Zadatku 1 odrediti potrebnu termičku otpornost hladnjaka, na koji se montiraju sve poluprovodničke komponente u pretvaraču. Usvojiti da je za ispravljačke elemente $V_{TO}=1V$, $r_D=5m\Omega$. Pretpostaviti temperaturni radni opseg $-25^{\circ}C...+60^{\circ}C$ i maksimalnu temperaturu na poluprovodničkim spojevima od $T_j=130^{\circ}C$. Nakon odabira hladnjaka izračunati temperaturu na kućištu modula temperaturu na hladnjaku.


3. Zadatak

Dimenzionisati komponente impulsnog pojačavača (Slika 1) za energetski tiristor 100A/1200V- PDT 10012 koji se koristi za početno punjenje elektrolita u Zadatku 1. Pojačanje tranzistora Q1 je $h_{FE}=40$; $V_{BES}=0.7V$ i $V_{CES}=0.2V$. Prenosni odnos optokaplera OC je $I_C/I_F=10$. Napon napajanja pojačavača je $E=12V$. Ulagi signal je pravougaoni impuls amplitude 5V. Pretpostaviti da forsirano uključenje tiristora traje $50\mu s$.

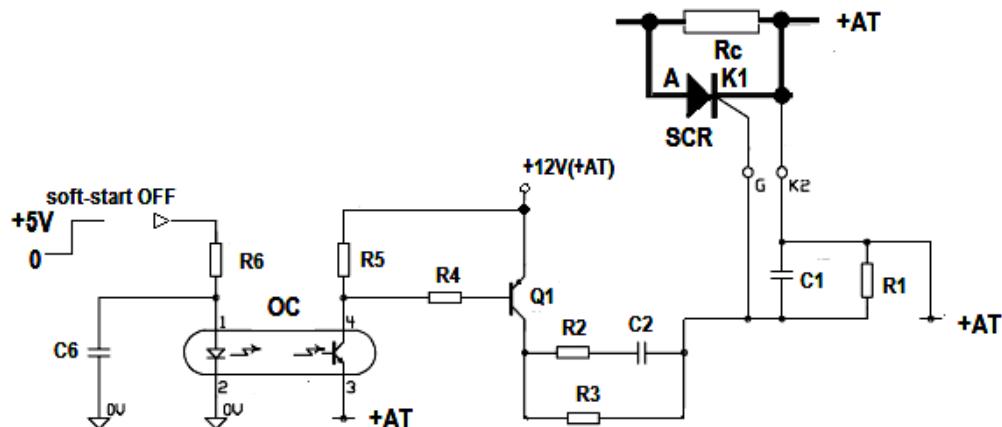

Slika1- pobudno SCR kolo

PRILOG 1

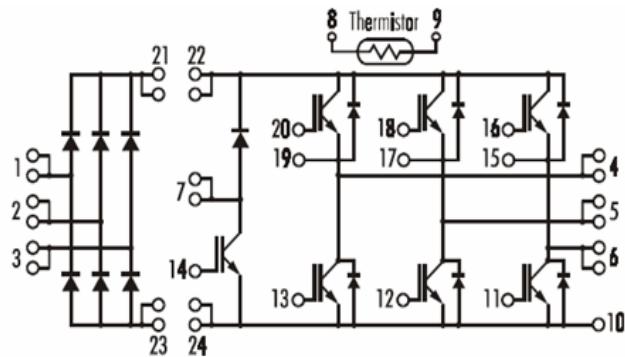



Absolute Maximum Ratings ($T_c=25^\circ\text{C}$)

	Items	Symbols	Test Conditions	Ratings	Units
Inverter	Collector-Emitter Voltage	V_{CES}		1200	V
	Gate -Emitter Voltage	V_{GES}		± 20	
	Collector Current	I_C	Continuous $25^\circ\text{C} / 80^\circ\text{C}$	75 / 50	A
Rectifier	I_C PULSE		1ms $25^\circ\text{C} / 80^\circ\text{C}$	150 / 100	
	- I_C PULSE			50	
	Collector Power Dissipation	P_C	1 device	360	W
Brake Chopper	Repetitive Peak Reverse Voltage	V_{RRM}		1600	V
	Average Output Current	I_O	50Hz/60Hz sinus wave	50	A
	Surge Current (Non Repetitive)	I_{FSM}	$T_j=150^\circ\text{C}, 10 \text{ ms, sinus wave}$	520	A
Brake Chopper	I_t (Non Repetitive)			1352	A's
	Collector-Emitter Voltage	V_{CES}		1200	V
	Gate -Emitter Voltage	V_{GES}		± 20	
Brake Chopper	Collector Current	I_C	Continuous $25^\circ\text{C} / 80^\circ\text{C}$	35 / 25	A
	I_C PULSE		1ms $25^\circ\text{C} / 80^\circ\text{C}$	70 / 50	
	Collector Power Dissipation	P_C	1 device	180	W
Brake Chopper	Repetitive Peak Reverse Voltage	V_{RRM}		1200	V
	Operating Junction Temperature	T_j		+150	$^\circ\text{C}$
	Storage Temperature	T_{Stg}		-40 ~ +125	
Brake Chopper	Isolation Voltage	V_{ISO}	A.C. 1min.	2500	V
	Mounting Screw Torque*			3.5	Nm


Thermal Characteristics

Items	Symbols	Test Conditions	Min.	Typ.	Max.	Units
Thermal Resistance (1 device)	$R_{th(j-c)}$	Inverter IGBT		0.35		$^\circ\text{C/W}$
		Inverter FRD		0.75		
		Brake IGBT		0.69		
		Rectifier Diode		0.50		
Contact Thermal Resistance	$R_{th(c-s)}$	With Thermal Compound	0.05			

PRILOG 2

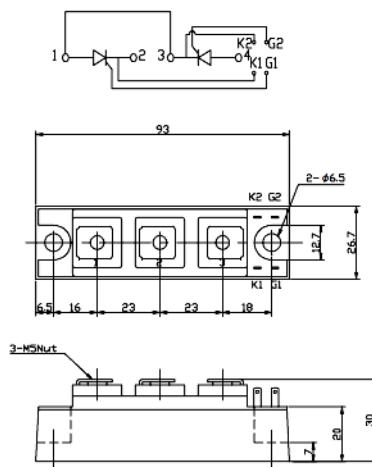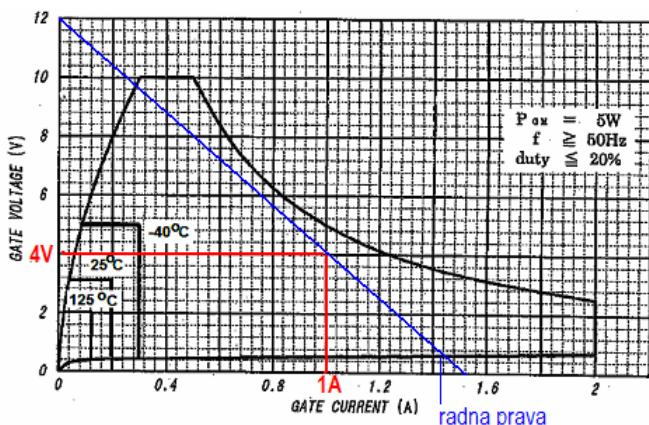

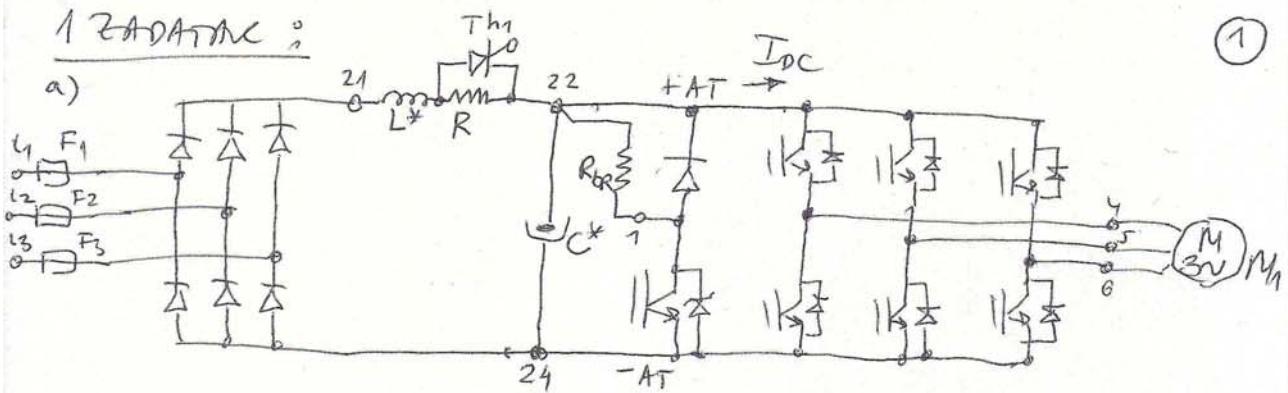Tehnički podaci: $V_{DRM}=1200\text{V}$, $I_{oAVG}=100\text{A}$, $I_{oRMS}=150\text{A}$; $IGT=200\text{mA}$, $V_{GT}=4\text{V}$; $R_{th(j-c)}=0.35\text{K/W}$, $R_{th(c-s)}=0.2\text{K/W}$



b) IZLAZNA SIRINA IGBT INVERTER JE $I_c = 50A$ (NOMINACNA SIRINA NA $80^\circ C$)

$$2P_{\text{mot}} [\text{kw}] \approx I_c [\text{A}] , \text{ or } P_{\text{mot}}^{\text{max}} = \frac{50}{2} = 25 \text{ kw}$$

Установлено, что на изучение и разработку проектов финансирования

PROF. MOTOR M_1 22 kW; 400 V, 50 Hz; $\eta = 99.2\%$; $\cos \varphi = 0.85$

$$P_{ee}^{MOT} = \frac{P_{MOT}}{7} = \frac{22 \text{ kW}}{0,92} = 23,9 \text{ kW}$$

$$I_{\text{mot}} = \frac{P_{\text{ee}}^{\text{Mot}}}{\sqrt{3}U \cdot \cos\varphi} = \frac{23,9 \text{ kW}}{\sqrt{3} \cdot 0,94 \text{ kV} \cdot 0,85} = 414 < 50 \text{ A}$$

)

NANON DC MECH-KOLP

$$U_{DC} = \frac{3V_m}{\pi} \quad V_m = 400\sqrt{2} \quad U_{DC} = \frac{3 \cdot 400\sqrt{2}}{\pi} = 538,8V^*$$

* ZANEMARENZE NA BID AUF DE PAKET WAREN IT ISPR. IN MÜHL.

$$P_{DC} = V_{DC} I_{DC} \quad P_{DC} \cdot \gamma_{inv} = P_{ee}^{MOT} \Rightarrow P_{DC} = \frac{P_{ee}^{MOT}}{\gamma_{inv}} = P_{ee}^{inv} + P_{ek}^{inv}$$

NA OSNOVU TABELE U PRLOM 1 uzbici u inverziju su

$$P_{je}^{inv} = 360 \text{ W}, \quad \text{verschiedene } P_{je*}^{inv} = 400 \text{ W}$$

$$P_{DC} = P_{ee}^{MOT} + P_{pe}^{inv} = 23,9 \text{ kW} + 0,4 \text{ kW} = 24,3 \text{ kW}$$

$$I_{DC} = \frac{24,3 \text{ kW}}{538,8 \text{ V}} = 45,1 \text{ A}$$

(2)

$$\Delta n_i \leq 2\% \quad \delta n_i \leq 10\%$$

zur Widerstand σ

$$C \geq \frac{1}{n \cdot \omega \cdot R_{\text{tot eur}}} \cdot \frac{\delta n_i}{\Delta n_i}$$


$$n = 6 \text{ (6 Pulsfrequenzsprünge)}$$

$$\omega = 2\pi f = 2\pi \cdot 50 \text{ Hz} = 314 \text{ rad/s}$$

$$\text{Rechnung} = \frac{U_{DC}}{I_{DC}} = \frac{538,8}{45,1} = 11,95 \Omega$$

$$C \geq \frac{1}{6 \cdot 314 \cdot 11,95} \cdot \frac{10}{2} = 222 \mu F \xrightarrow{\text{nehmen}} C^* = 250 \mu F / \text{Kvar}$$

Batteriebank

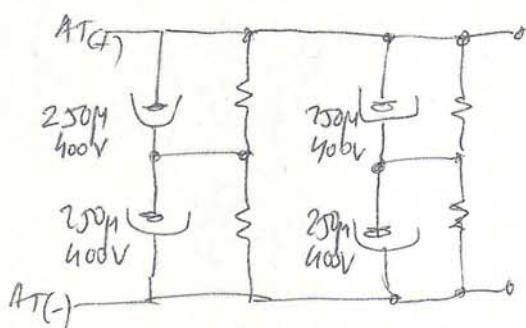

NAPOMENA:
MOŽE SE USVOJIT

$$; \text{ widerstand } C^{**} = 330 \mu F / \text{Kvar}$$

$$\text{Widerstand Induktivität} \quad L_{UR} = \frac{R_{\text{tot eur}}}{105 \omega} = \frac{11,95}{105 \cdot 314} = 0,36 \text{ mH}$$

Induktivität L :

$$L \geq \frac{1}{(6\omega)^2 C^*} \cdot \frac{4 R_{\text{tot eur}} \cdot 6\omega C^*}{35 \cdot \delta_i} + \frac{1}{(6\omega)^2 C^*}$$

$$\delta_i = \frac{\delta_i \%}{100} = \frac{10}{100} = 0,1$$

$$L \geq \frac{4 \cdot R_{\text{tot eur}}}{35 \cdot 6\omega \cdot \delta_i} + \frac{1}{(6\omega)^2 C^*}$$

$$L \geq \frac{4 \cdot 11,95}{35 \cdot 6 \cdot 314 \cdot 0,1} + \frac{1}{(6 \cdot 314)^2 \cdot 250 \mu F}$$

$$L \geq 7,25 \text{ mH} + 1,12 \text{ mH} = 8,37 \text{ mH} \xrightarrow{\text{nehmen}} L^* = 8,5 \text{ mH / 50A}$$

(3)

$$I_{DC} = 45,1A \quad \Delta I_{DC} = 0,1 I_{DC} = 0,1 \cdot 45,1 = 4,51A$$

$$I_{Cmax} = 45,1 + \frac{4,51}{2} = 47,4A \rightarrow \text{Maximales } I_{Cmax} = 50A$$




$$L^* = 8,5mH / 50A$$

REZONANZAUCHEITENWERT „LC“ FILTRA

$$\omega_{rez} = \frac{1}{\sqrt{L^* C^*}} = \frac{1}{\sqrt{8,5mH \cdot 0,75nF}} = 686 \text{ rad/s}$$

$$f_{rez} = \frac{\omega_{rez}}{2\pi} = \frac{686}{2\pi} = 109,2Hz$$

PRAEVANT F-NA „LC“ FILTRA

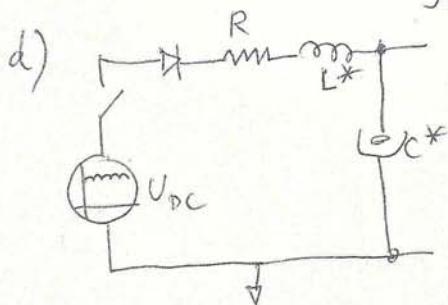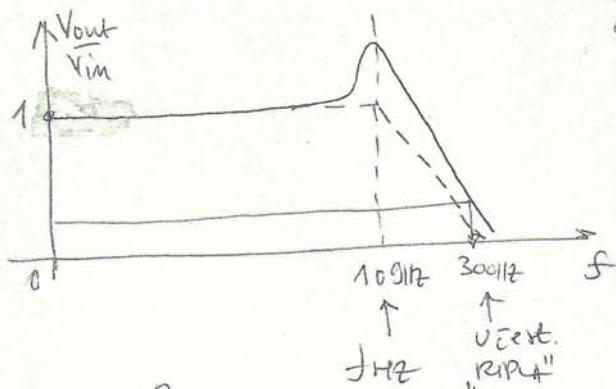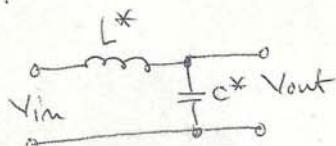

BEZ OPERATORKEIT R MAX 87mΩ
PUNZIGER WENNENWERT C JE:

$$I_{Cmax} = \frac{U_{DC}}{Z_C} = \frac{U_{DC}}{\sqrt{\frac{L^*}{C^*}}} = \frac{538,8}{\sqrt{8,5mH \cdot 0,75nF}}$$

$$I_{Cmax} = \frac{538,8}{5183} \approx 92,4A \approx 93A$$

OTVORANIE R JE BIKAT THRO AT ZADOVOLI KRIETENIN OPORNIV R_{UR} = 2\sqrt{\frac{L^*}{C^*}}

$$R_{UR} = 11,66\Omega \quad \text{UVORACENIE } R = 12\Omega$$

$$\text{SINTZE MAX. SINTA PUNZIGER } I_{Cmax}^1 = \frac{1,1 U_{DC}}{R + Z_C} = \frac{1,1 \cdot 538,8}{12 + 5,83}$$

$$I_{Cmax}^1 = \frac{593}{17,83} = 33,26A$$

ZA OKAMICENJE SINTA PUNZIGER OP 30A, NEBOZI RIBNRA

$$I_{Cmax}'' = 30A \quad \frac{1,1 U_{DC}}{R + Z_C} = 30 \quad R + Z_C = \frac{1,1 U_{DC}}{30} \Rightarrow R = \frac{1,1 U_{DC}}{30} - Z_C = 14\Omega$$

MUSRAJAMOR = 14\Omega / 100W


$$e) I_{DC} = 45,1 A$$

EFFECTIVE CURRENT
UNIDIRECTIONAL

$$I_{L\text{eff}} = \sqrt{\frac{2 I_{DC}^2 \cdot \frac{2\pi}{3}}{2\pi}}$$

$$I_{L\text{eff}} = \sqrt{\frac{2}{3}} I_{DC}$$
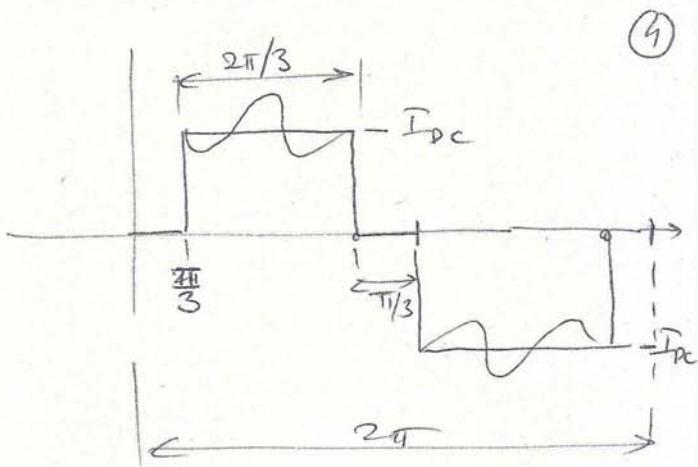
$$I_{L\text{eff}} = \sqrt{\frac{2}{3}} \cdot 45,1 = 36,8 A$$



- Maximum operating at 40A, voltage 650V
- Operating point BJT UNCLIPPER (UBO)

$$I_{t(\text{diode})}^2 \underset{18\mu R}{\geq} I_{t(\text{UBO})}^2$$

$$\text{Previous } I_{t(\text{diode})}^2 \approx 2 I_{t(\text{UBO})}^2$$

$$\Rightarrow I_{t(\text{UBO})}^2 = \frac{1}{2} I_{t(\text{diode})}^2 = \frac{1}{2} \cdot 1352 \text{ A}^2 \cdot \text{s}$$

$$I_{t(\text{UBO})}^2 \approx 670 \text{ A}^2 \cdot \text{s}$$

UBO:

$$40 \text{ A} / 650 \text{ V} ; 670 \text{ A}^2 \cdot \text{s}$$

$$f) P_{BR} \approx \frac{1,2 U_{DC}^2}{R_{BR}} \quad P_{BR} \approx P_{\text{mot}}^{\text{el}} = 23,9 \text{ kW}$$

$$R_{BR} = \frac{1,2 U_{DC}^2}{P_{BR}} = \frac{1,2 \cdot 538,8^2}{23,9 \text{ kW}} = 14,57 \Omega \rightarrow 15 \Omega$$

$$R_{BR} = 15 \Omega / 1 \text{ kW}_{\text{cont.}} \quad t_u \approx 1 \text{ s} \quad E = \frac{1,2 \cdot 538,8^2}{15 \Omega} \cdot 1 \text{ s} = 6,45 \text{ kWh}$$


2 ZADANIE

(5)

$$V_{TO} = 1V \quad r_d = 5 \text{ m}\Omega$$

$-25^\circ\text{C} \dots + 60^\circ\text{C}$ $T_{J,\max} = 130^\circ\text{C}$

EQUIVALENTE TERMICKA ŘEŠENÍ:

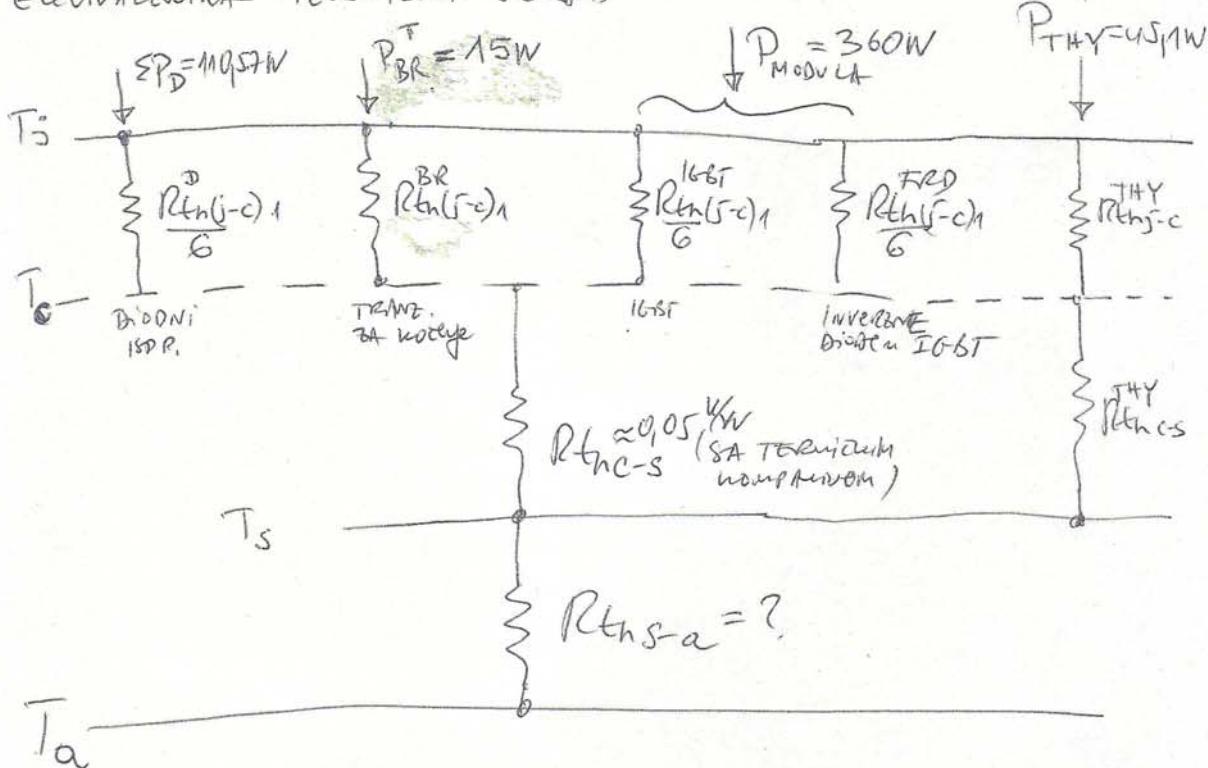

* $\sum P_D = 6 \cdot P_{D1}$ - můžeme si díky tomu i vypočítat

$$P_{D1} = V_{TO} I_{DSR} + V_D \cdot I_{Deff}^2 \quad I_{DSR} = \frac{I_{DC}}{3} = \frac{45.1}{3} = 15.034$$

$$P_{D1} = 1 \cdot 15.034 + 5 \cdot 10^{-3} \cdot 26.07^2 \quad I_{Deff} = \frac{I_{DC}}{\sqrt{3}} = \frac{45.1}{\sqrt{3}} = 26.074$$

$$P_{D1} = 18.42 \text{ W}$$

$$P_D = 6P_{D1} = 108.57 \text{ W}$$

* $P_{BR}^T \approx 60 \text{ W} \left(\frac{1}{6} \cdot 360 \text{ W} \right) \rightarrow$ obzírku DA je možné operovat
ne myslíme zde toto mnoho mít.

$$P_{BR}^T \approx 10 \div 20 \text{ W} (\text{máme } 15 \text{ W})$$

* $P_{modulator} = 360 \text{ W}$

$$\star P_{THY} = V_{TO} \cdot I_{DC} = 1 \cdot 45,1 \approx 45,1 \text{ W}$$

(6)

Umaas Smit Disipate svit elementen te berekenen de


$$\Sigma P_{dis} = \Sigma P_D + P_{BR}^+ + P_{modula} + P_{THY}$$

$$= 110,57 \text{ W} + 15 \text{ W} + 360 \text{ W} + 45,1 \text{ W} = 530,67 \text{ W}$$


Moeilijkheid DA te zodat doort mit berekent u stappen

$$\Sigma P_{dis}^* = 550 \text{ W}$$


Equiv. reductie reet de

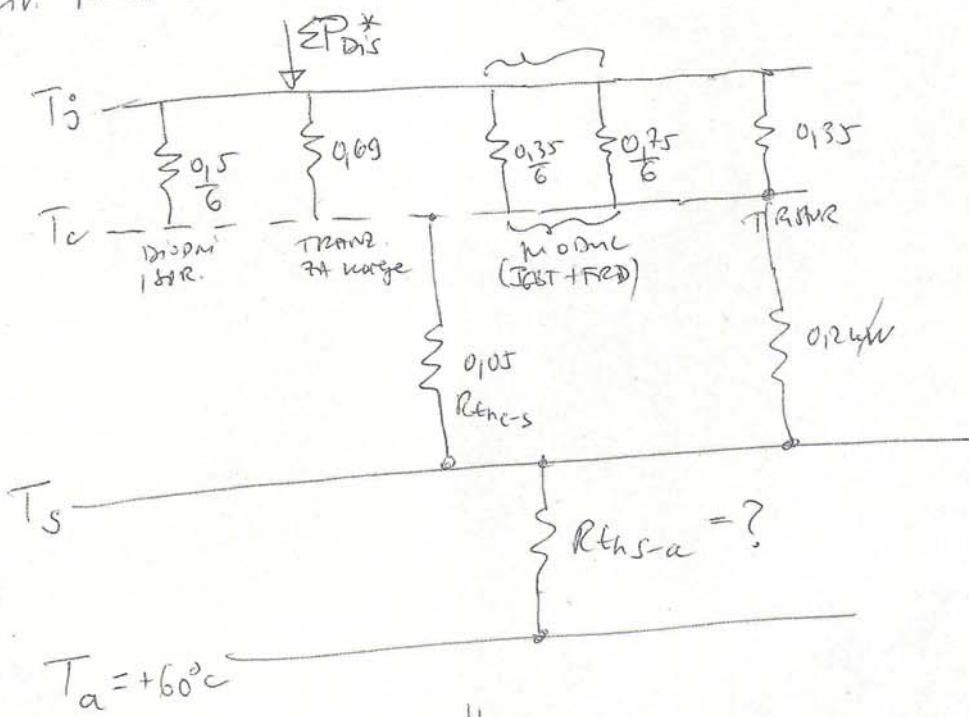

$$T_a = +60^\circ\text{C}$$

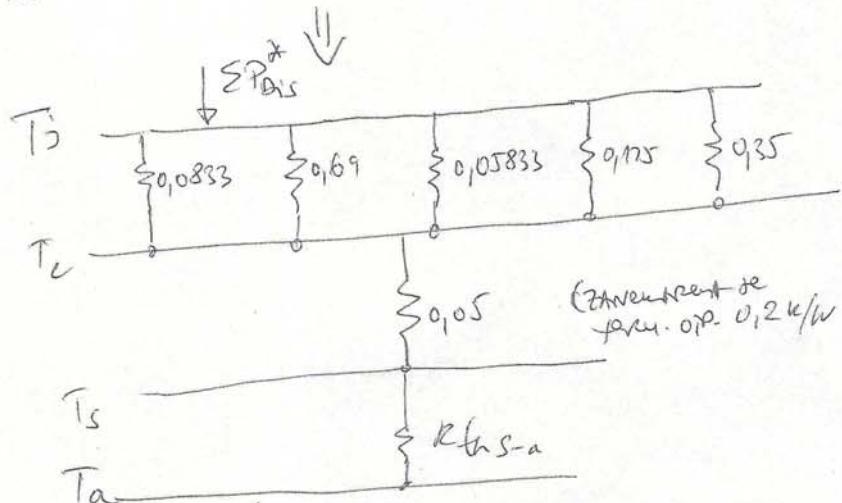

(7)

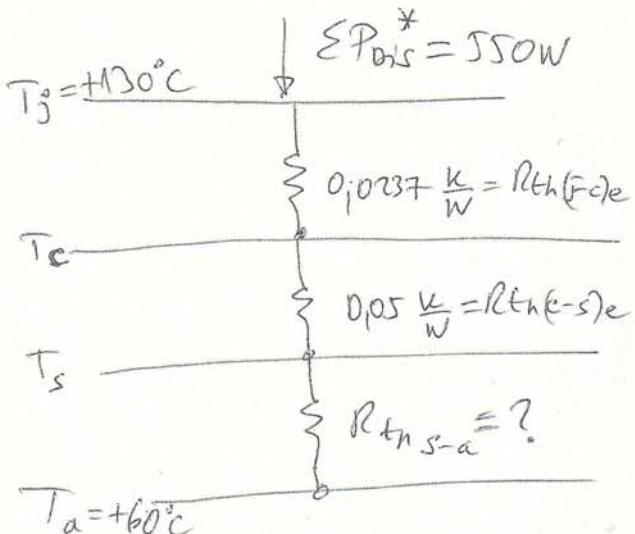

$$R_{th}(s-a) + R_{th}(f-c)_e + R_{th}(c-s)_e < R_{th}^*$$

$$R_{th}^* = \frac{T_{j\max} - T_{a\max}}{\Sigma P_{DSS}^*}$$

$$R_{th}(s-a) + R_{th}(f-c)_e + R_{th}(c-s)_e < \frac{T_{j\max} - T_{a\max}}{\Sigma P_{DSS}^*}$$

$$R_{th}(s-a) + 0,0237 + 0,05 < \frac{130^\circ - 60^\circ}{550W}$$

$$R_{th}(s-a) < \frac{130 - 60}{550} = 0,0237 - 0,05$$

$$R_{th}(s-a) < 0,127 - 0,0237 - 0,05 = 0,0535 \frac{k}{W} (\frac{^\circ C}{W})$$

Uzvoříme si že $R_{th}(s-a) = 0,05 \frac{k}{W}$

- TEMPERATURA HLAZNÍKU NA OVN MÁVÍME VLOMOŠT JE:

$$T_S = T_a + R_{th}(s-a) \cdot \Sigma P_{DSS}^* = 60^\circ C + 0,05 \cdot 550 = 87,5^\circ C$$


- TEMPERATURA NA KUCHYŇSKÉM MĚŘIDLE

$$T_C = T_S + R_{th}(c-s)_e \cdot \Sigma P_{DSS}^* = 87,5^\circ C + 0,05 \cdot 550$$

$$T_C = 115^\circ C$$

3 zadanie

(8)

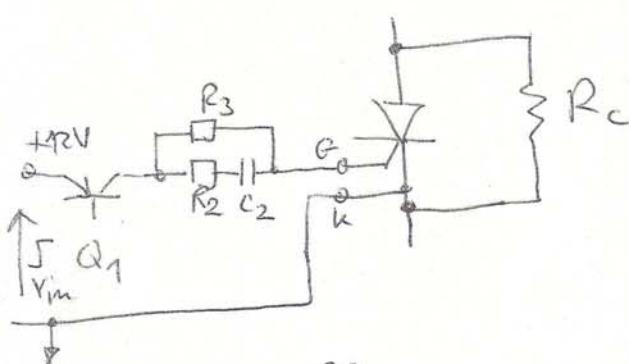


$$V_{BES} = 0,7V$$

$$V_{CEJ} = 0,2V$$


$$h_{FE} = 40$$

$$I_d/I_F = 60$$

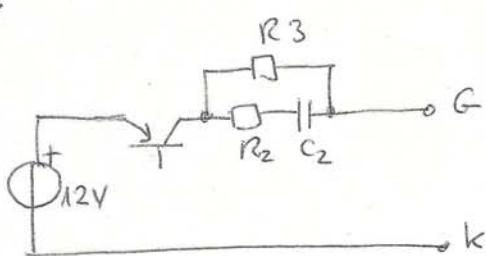
NA OSNOVE DIZAJNU JE
PREDLOGA 2 UZVODJENO DA JE
FUNKCIJALNI GRADJEĆI GEM I_G^{*} = 1A


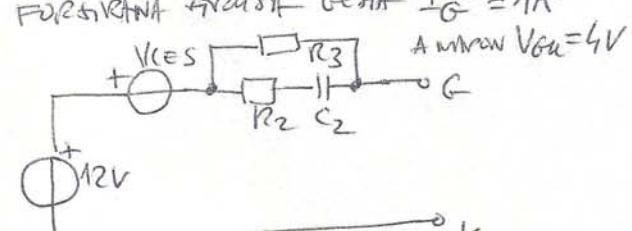
$$\Rightarrow \begin{cases} +12V \\ -12V \end{cases}$$



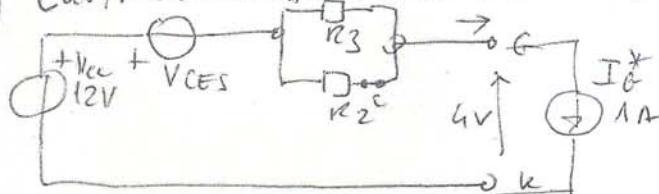4) EKVIV. ŠEMA ZA FORSIKANI MEDIJ (NA SREDNJI VRED. ZE, US")



$$V_{cc} = V_{ces} + (R_3 \parallel R_2) I_G^* + V_{ok}$$


$$I_G^* = \frac{V_{cc} - V_{ces} - V_{ok}}{R_2 \parallel R_3}$$

$$I_G^* = \frac{V_{cc} - V_{ces} - V_{ok}}{R_2 R_3}$$

$$\frac{R_2 R_3}{R_2 + R_3} = \frac{V_{cc} - V_{ces} - V_{ok}}{I_G^*} = \frac{12 - 0,2 - 4}{1A} = 7,8 \Omega$$

$$\boxed{\frac{R_2 R_3}{R_2 + R_3} = 7,8 \Omega}$$

B) EKVIV. ŠEMA ZA "USTVORENI REZI"

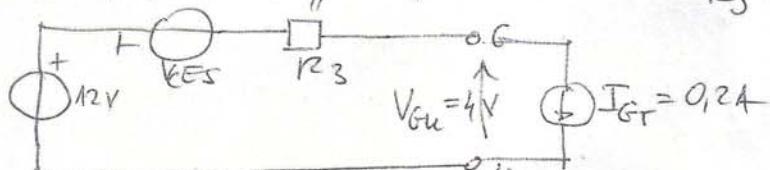


$$R_3 = \frac{V_{cc} - V_{ces} - V_{ok}}{I_G}$$

$$R_3 = \frac{12 - 0,2 - 4}{0,2} = 40 \Omega$$




$$R_3 = 39 \Omega$$

$$\frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{7,8} \Rightarrow \frac{1}{R_2} = \frac{1}{7,8} - \frac{1}{40} = 0,128 - 0,0256 = 0,1023$$
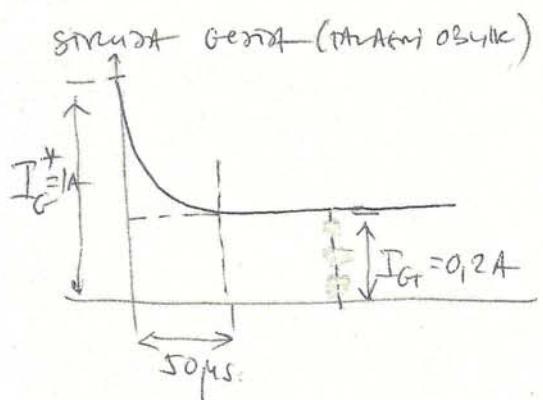
$$R_2 = 9,76 \Rightarrow R_2 = 10 \Omega$$



$$I_2 = 1A - 0,2A = 0,8A$$

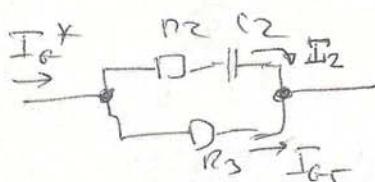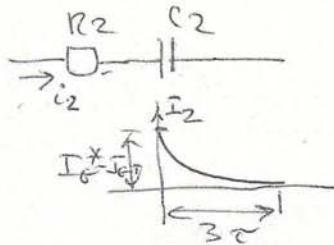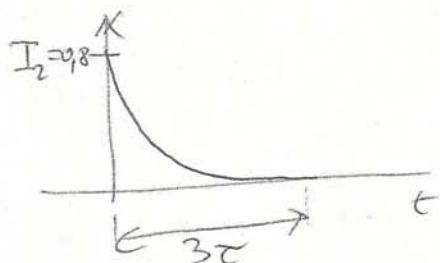

$$I_2 + I_{GT} = I_C^*$$

$$i_2 = I_2 e^{-\frac{t}{\tau}}$$

$$3\tau = 50\mu s$$

$$3 \cdot R_2 C_2 = 50\mu s \quad R_2 C_2 = \frac{50}{3}\mu s$$

$$C_2 = \frac{50}{3}\mu s \cdot \frac{1}{R_2} = \frac{50}{3} \cdot \frac{1}{10} \mu F = 1,66 \mu F$$

Dissipacija u R₂:

$$P_{R2} = R_2 I_{R2}^2 = 10 \cdot 0,8^2 = 10,98 W$$


~~P_{R2} = 6,4 W (u trazanju ≈ 50μs)~~ Možete da $\boxed{C_2^* = 2,2 \mu F}$

Dissipacija u R₃:

$$P_{R3} = R_3 I_{R3}^2 = 30 \cdot 0,2^2 = 1,56 W$$

* PROJEKCIUN OPORNICKA R_4, R_S, R_G

(10)

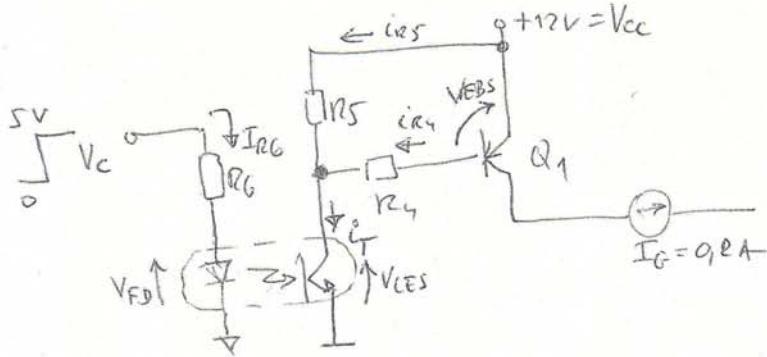

$$V_C = R_G I_{R_G} + V_{FD}$$

V_{FD} - NAPRVN NA (ED) OBDOB
OPNUVARETA

$$V_{FD} = 1,2 \text{ V}$$

$$V_C = 5 \text{ V} \quad V_{FD} = 1,2 \text{ V}$$

$$I_{R_G} = 2 \mu\text{A} \text{ (usvozeno)}$$

$$R_G = \frac{V_C - V_{FD}}{I_{R_G}} = \frac{5 - 1,2}{2 \mu\text{A}} = 1,9 \text{ k.}$$

$$\boxed{R_G^* = 2 \text{k} / 0,25 \text{W}}$$

OPNUV OC

$$I_T = \left(\frac{I_C}{I_F} \right) \cdot I_{R_G}$$

$$I_T = 10 \cdot 2 \mu\text{A} = 20 \mu\text{A}$$

$$i_{R_4} = \frac{I_C}{h_{FE}} = \frac{I_G}{h_{FE}} = \frac{0,12}{40} = 5 \mu\text{A}$$

$$i_{R_S} + i_{R_4} = i_T$$

$$i_{R_S} = i_T - i_{R_4} = 20 \mu\text{A} - 5 \mu\text{A}$$

$$i_{R_S} = 15 \mu\text{A}$$

$$V_{CC} = R_S i_{R_S} + V_{CES}$$

$$\frac{V_{CC} - V_{CES}}{i_{R_S}} = R_S$$

$$R_S = \frac{12 - 0,2}{15 \mu\text{A}} = 786 \Omega$$

$$\text{Mnemo} \boxed{R_S^* = 1 \text{k} / 0,25 \text{W}}$$

$$V_{CC} = V_{EBSS} + R_4 i_{R_4} + V_{CES}$$

$$V_{CC} = \underbrace{V_{EBSS}}_{0,7 \text{V}} + R_4 i_{R_4} + 0,2 \text{V}$$

$$\frac{12 - 0,7 - 0,2}{i_{R_4}} = R_4$$

$$\frac{11,1}{i_{R_4}} = R_4 \Rightarrow \frac{11,1}{5 \mu\text{A}} = 2 \text{k}\Omega$$

$$R_4 = 2 \text{k}\Omega \quad P_{R_4} = 2 \text{k}\Omega \cdot (5 \mu\text{A})^2 = 0,055 \text{W}$$

$$\boxed{R_4^* = 2 \text{k}\Omega / 0,25 \text{W}}$$